

# LENGUAJE DE DESCRIPCION DE HARDWARE





# LENGUAJE DE DESCRIPCION DE HARDWARE

## Percentage of FPGA Study Participation by Region



Source: Wilson Research Group and Mentor Graphics, 2014 Functional Verification Study

# LENGUAJE DE DESCRIPCION DE HARDWARE

 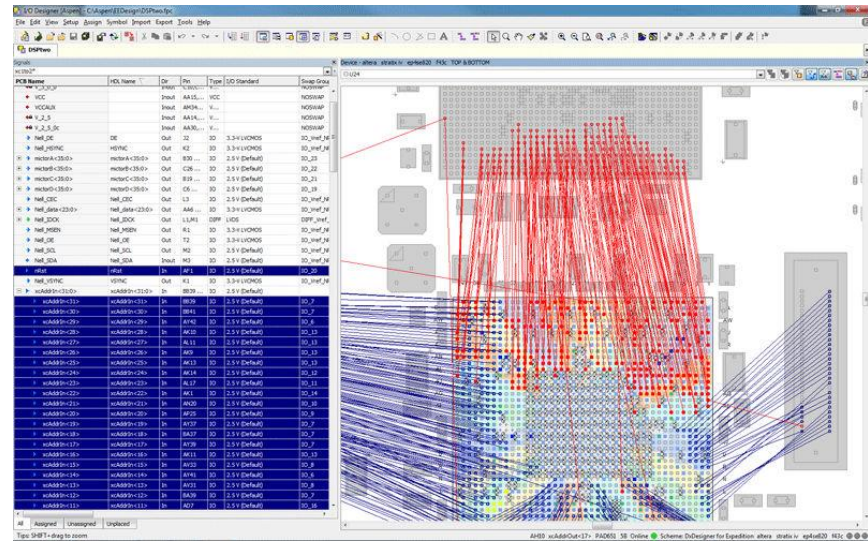

# Dispositivos Programables



(a) Programmable read-only memory (PROM)



(b) Programmable array logic (PAL)



(c) Programmable logic array (PLA)


**FIGURE 7.13**

Basic configuration of three PLDs

# PLA

$$F_1 = AB' + AC + A'BC'$$


$$F_2 = (AC + BC)'$$

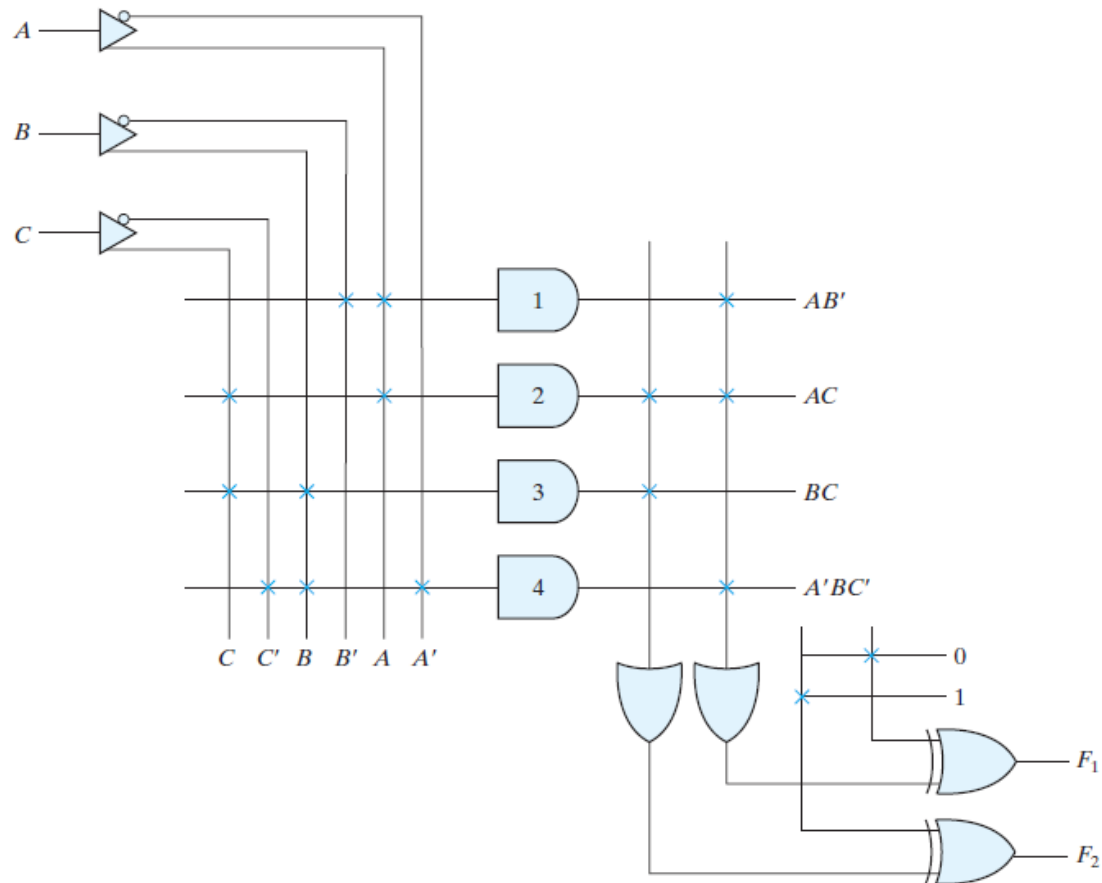

**FIGURE 7.14**

PLA with three Inputs, four product terms, and two outputs

# PAL

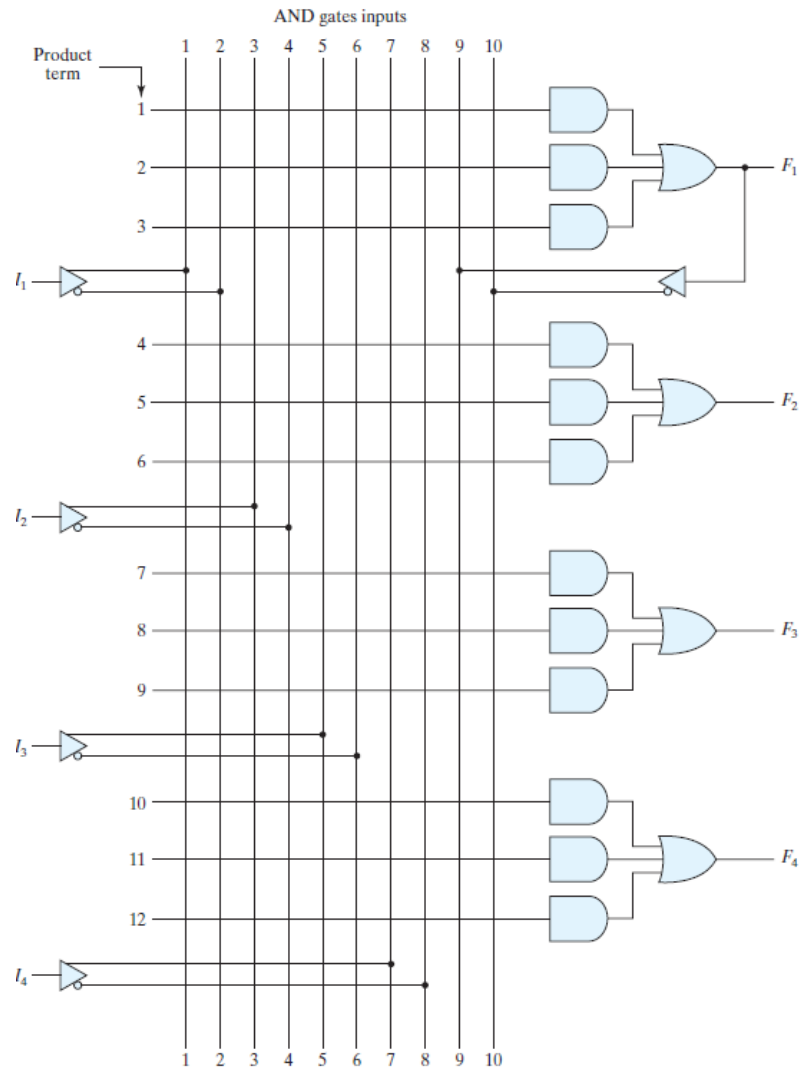


**FIGURE 7.16**  
PAL with four inputs, four outputs, and a three-wide AND-OR structure

# PAL


**Table 7.6**  
*PAL Programming Table*

Product Term	AND Inputs					Outputs
	A	B	C	D	w	
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$x = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	$y = A'B + CD + B'D'$
7	0	1	—	—	—	
8	—	—	1	1	—	
9	—	0	—	0	—	$z = w + AC'D' + A'B'C'D$
10	—	—	—	—	1	
11	1	—	0	0	—	
12	0	0	0	1	—	

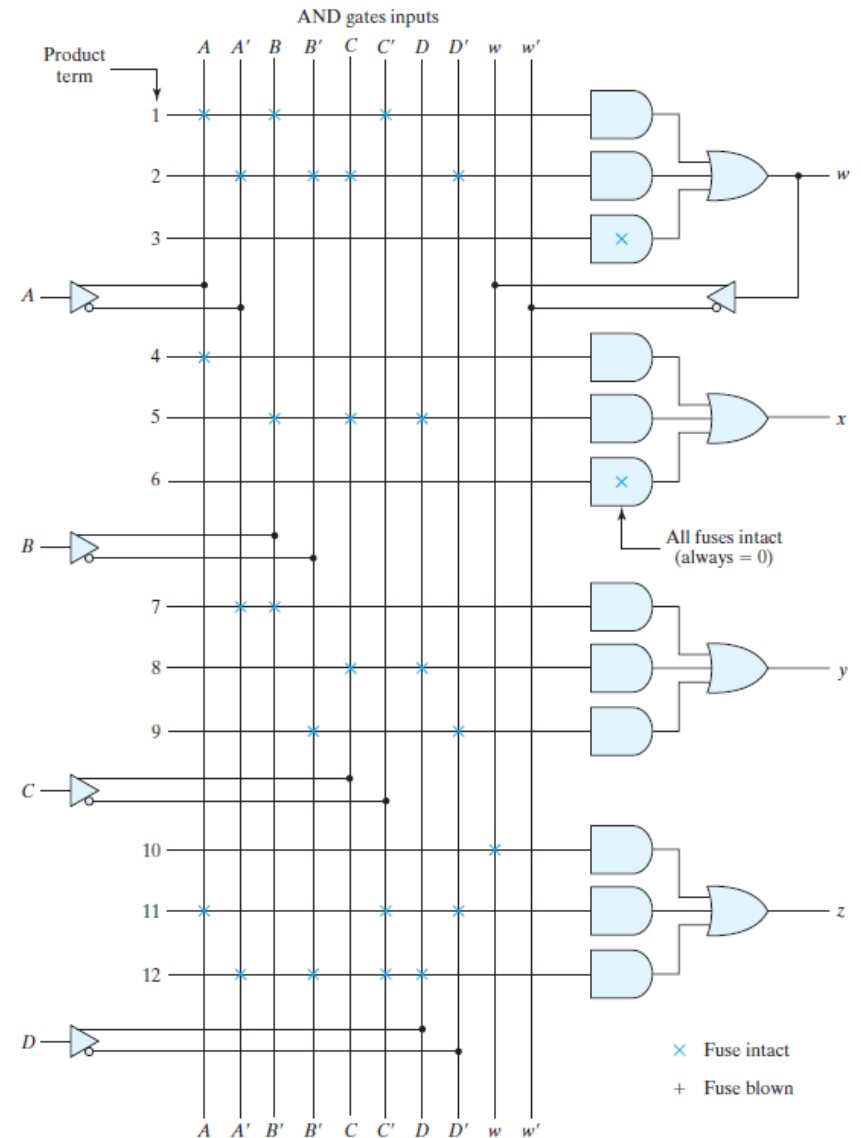


**FIGURE 7.17**  
Fuse map for PAL as specified in Table 7.6

## SPLD - CPLD- FPGA

 


**FIGURE 7.18**  
Sequential programmable logic device

 

**FIGURE 7.19**  
Basic macrocell logic




## SPLD - CPLD- FPGA

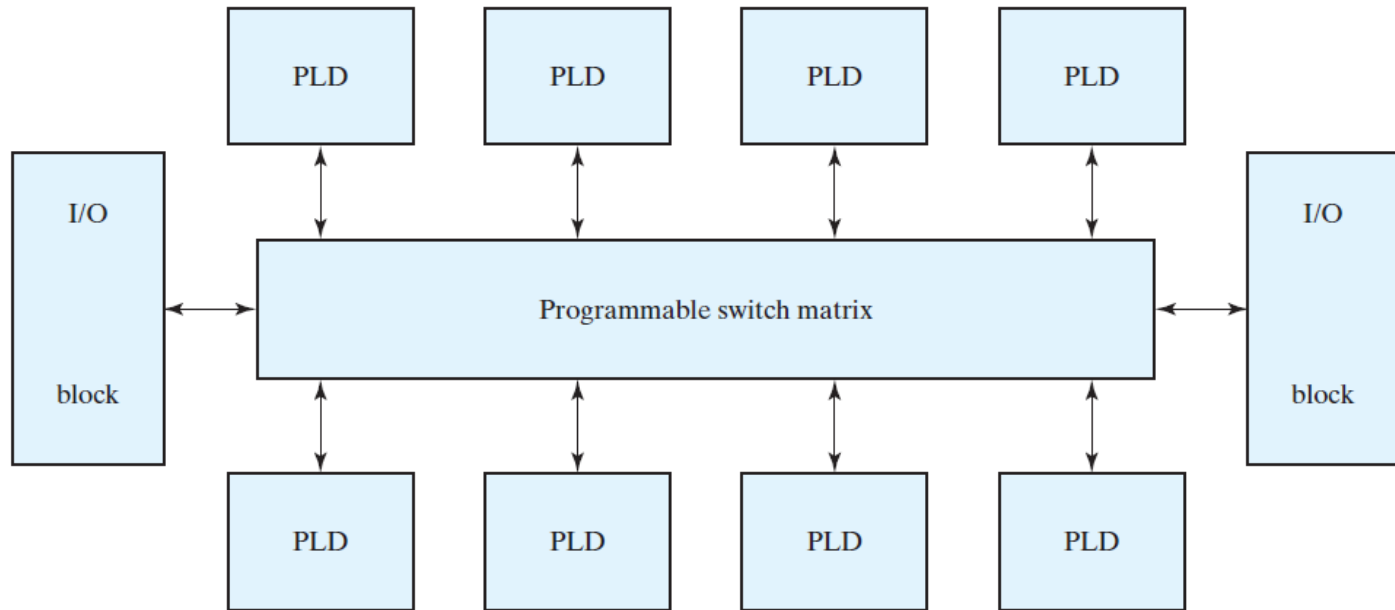


**FIGURE 7.20**  
General CPLD configuration
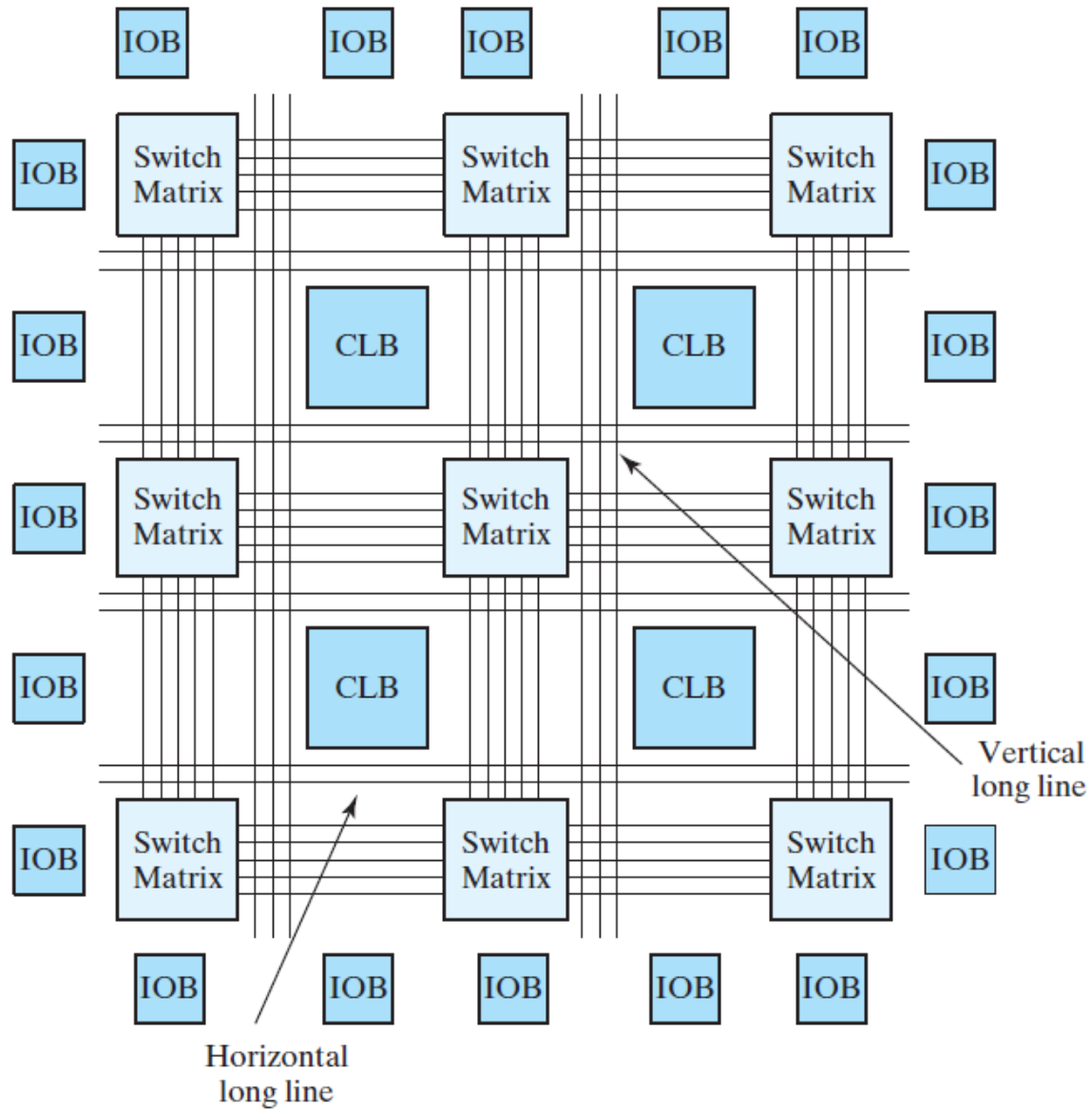
# FPGA




# FPGA - CLB

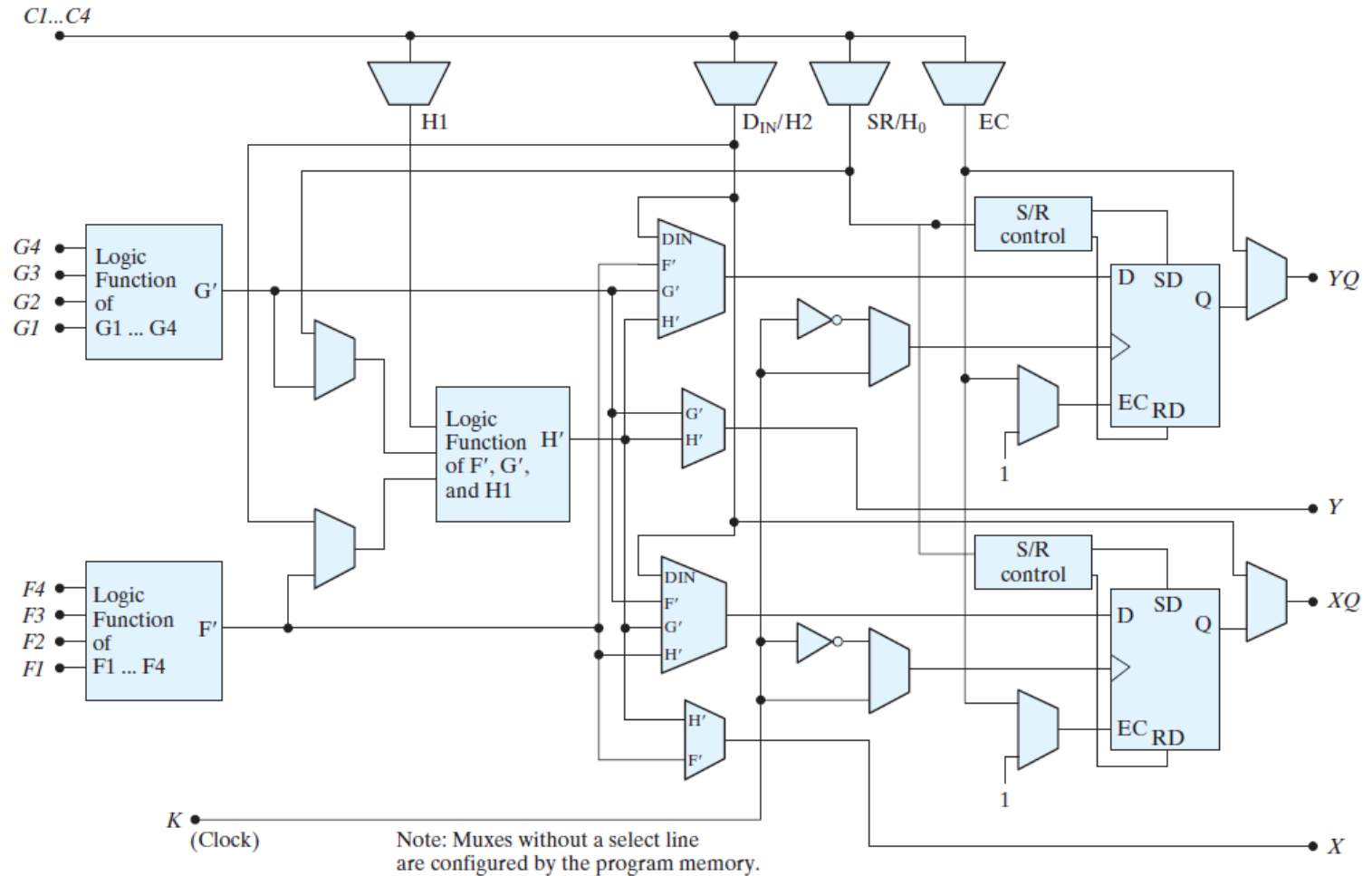


**FIGURE 7.22**  
CLB architecture

## FPGA – Block RAM

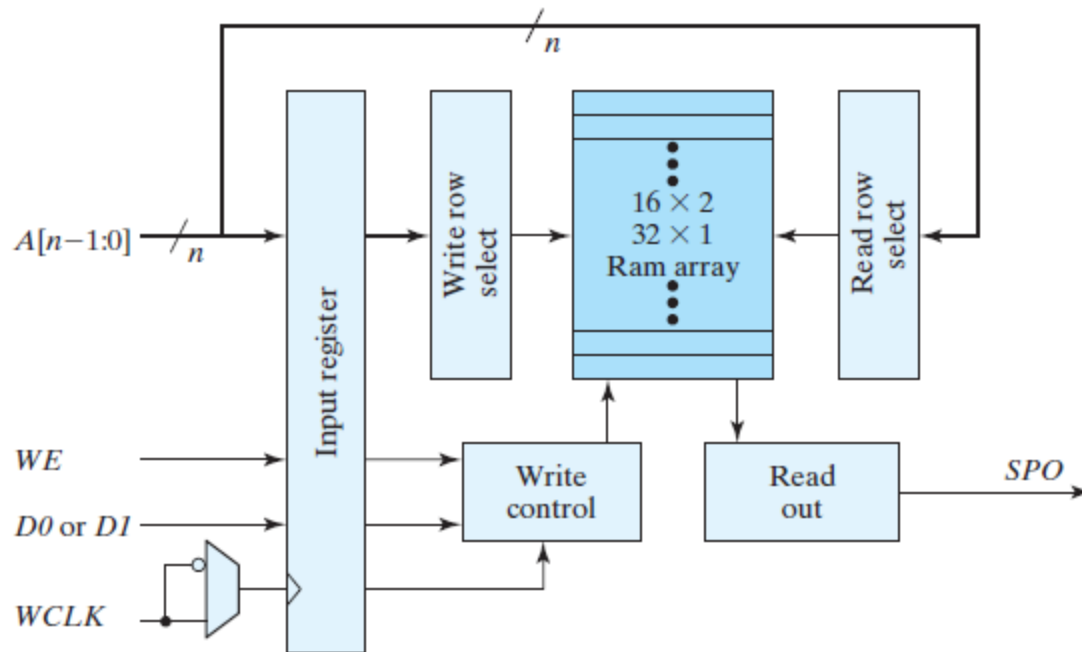


**FIGURE 7.26**  
Distributed RAM cell formed from a lookup table

## FPGA – Block RAM Dual Port

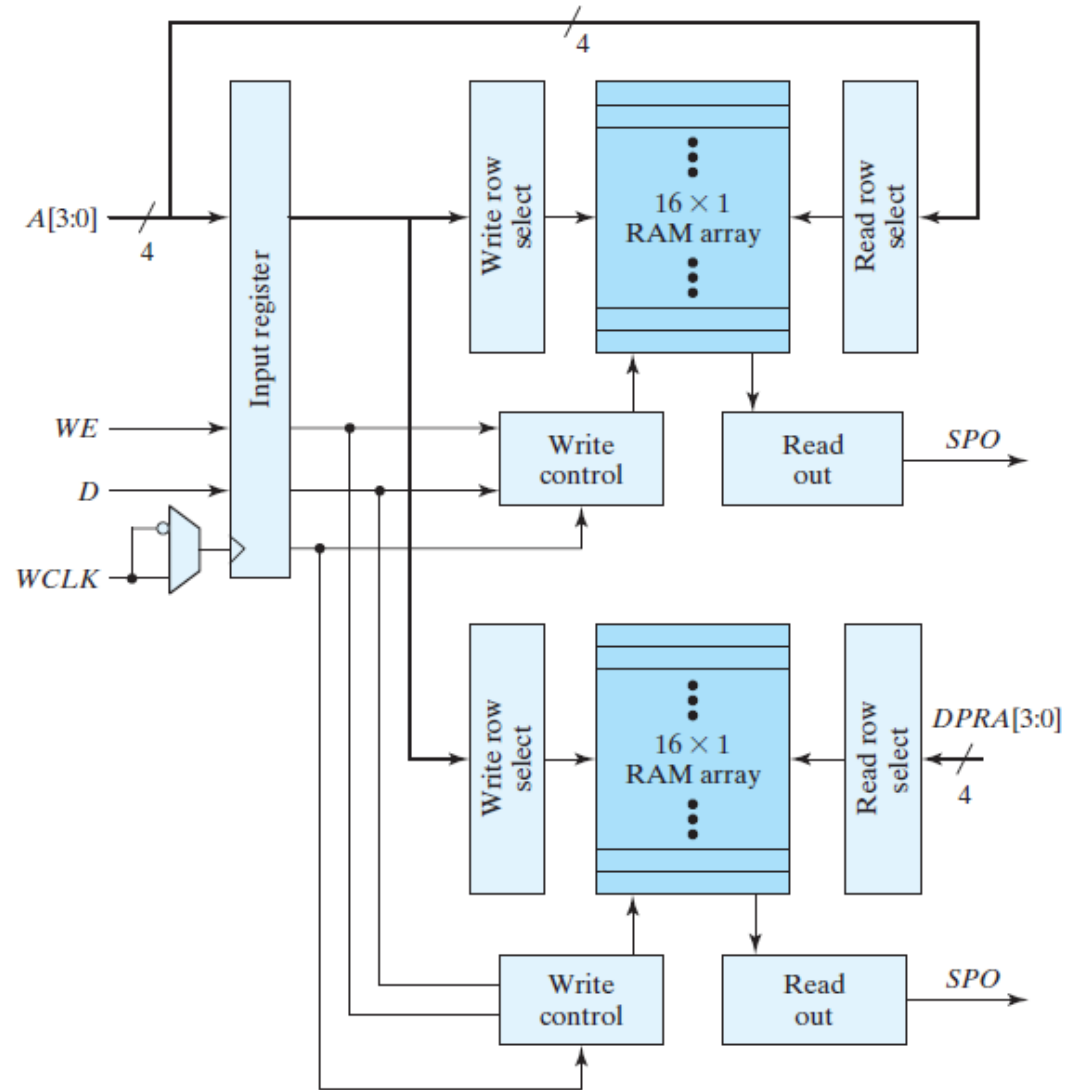


**FIGURE 7.27**  
Spartan dual-port RAM

# FPGA

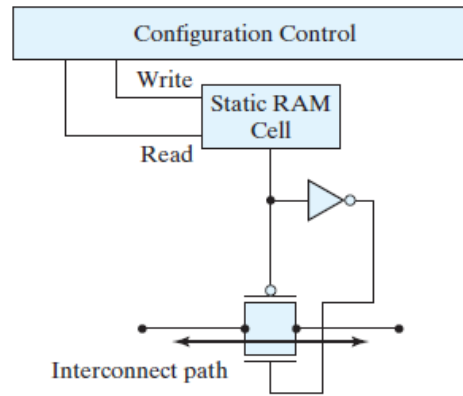


**FIGURE 7.23**  
RAM cell controlling a PIP transmission gate

 

**FIGURE 7.24**  
Circuit for a programmable PIP

## FPGA - IOB

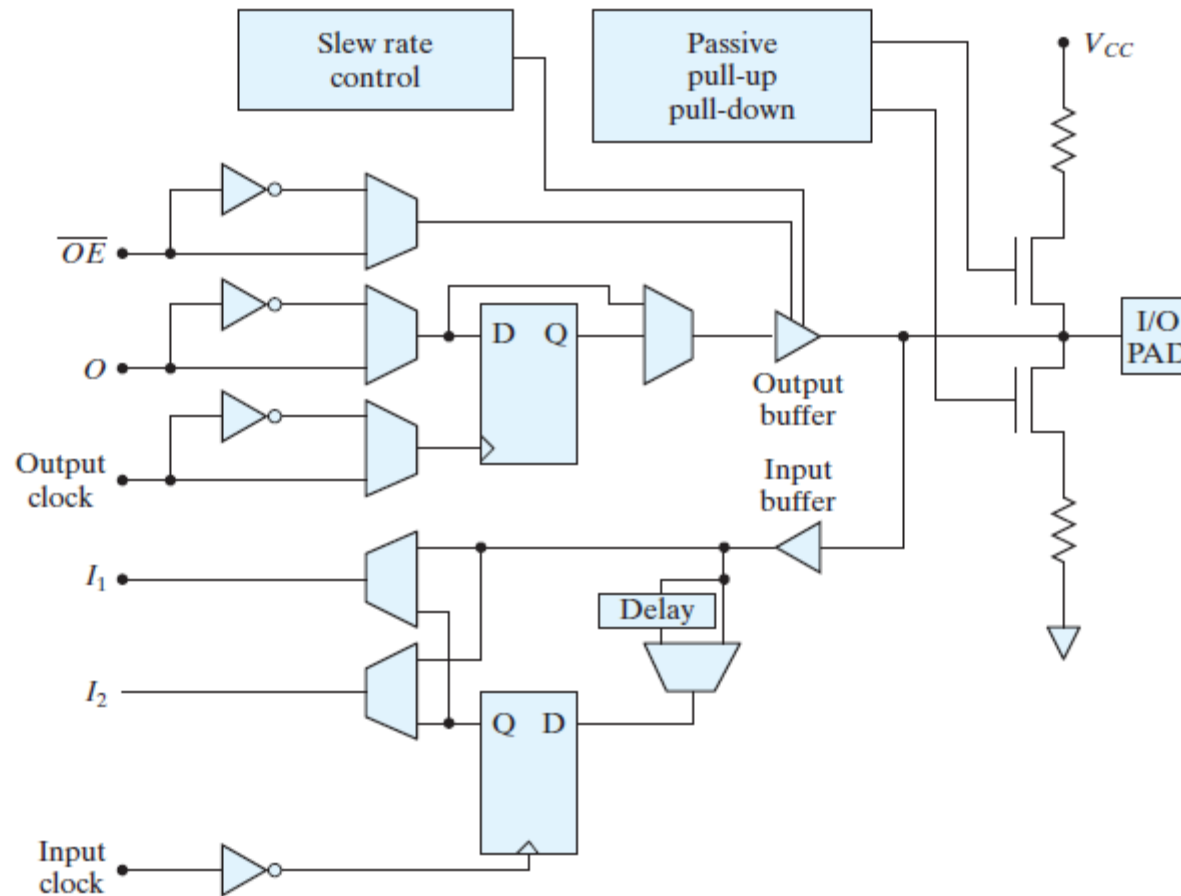

**FIGURE 7.25**  
XC4000 series IOB

# FPGA - IOB

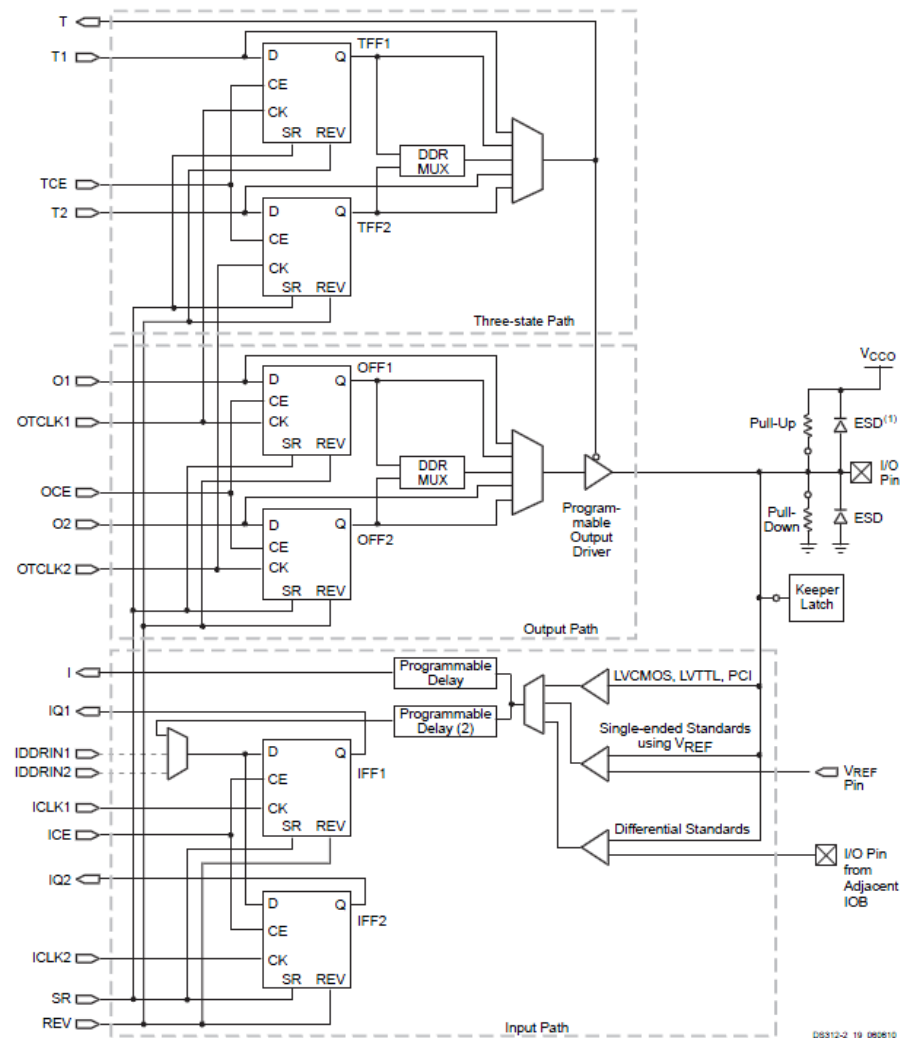


Figure 10-1: Simplified IOB Diagram



# FPGA - IOB

 


Figure 10-5: Output Buffer (OBUF) Symbol

 


Figure 10-6: 3-State Output Buffer (OBUFT) Symbol

 


Figure 10-7: Input/Output Buffer (IOBUF) Symbol

 


Figure 10-3: Global Clock Input Buffer (IBUFG) Symbol

 


Figure 10-4: Differential Input Buffer (IBUFDS) Symbol

```
-- INOUT_PORT : inout STD_LOGIC;
--**Insert the following between the
-- 'architecture' and 'begin' keywords**
signal IN_SIG, OUT_SIG, T_ENABLE: std_logic;
component IOBUF
    port (I, T: in std_logic;
          O: out std_logic;
          IO: inout std_logic);
end component;
--**Insert the following after the 'begin' keyword**
U1: IOBUF port map (I => OUT_SIG, T => T_ENABLE,
                    O => IN_SIG, IO => INOUT_PORT);
```

# FPGA


**Table 7.8**  
*Spartan II Device Attributes*

<b>Spartan II FPGAs</b>	<b>XC2S15</b>	<b>XC2S30</b>	<b>XC2S50</b>	<b>XC2S100</b>	<b>XC2S150</b>	<b>XC2S200</b>
System Gates <sup>1</sup>	6K–15K	13K–30K	23K–50K	37K–100K	52K–150K	71K–200K
Logic Cells <sup>2</sup>	432	972	1,728	2,700	3,888	5,292
Block RAM Bits	16,384	24,576	32,768	40,960	49,152	57,344
Max Avail I/O	86	132	176	196	260	284

<sup>1</sup>20–30% of CLBs as RAM.


<sup>2</sup>1 Logic cell = four-input lookup table + flip-flop.

# FPGA

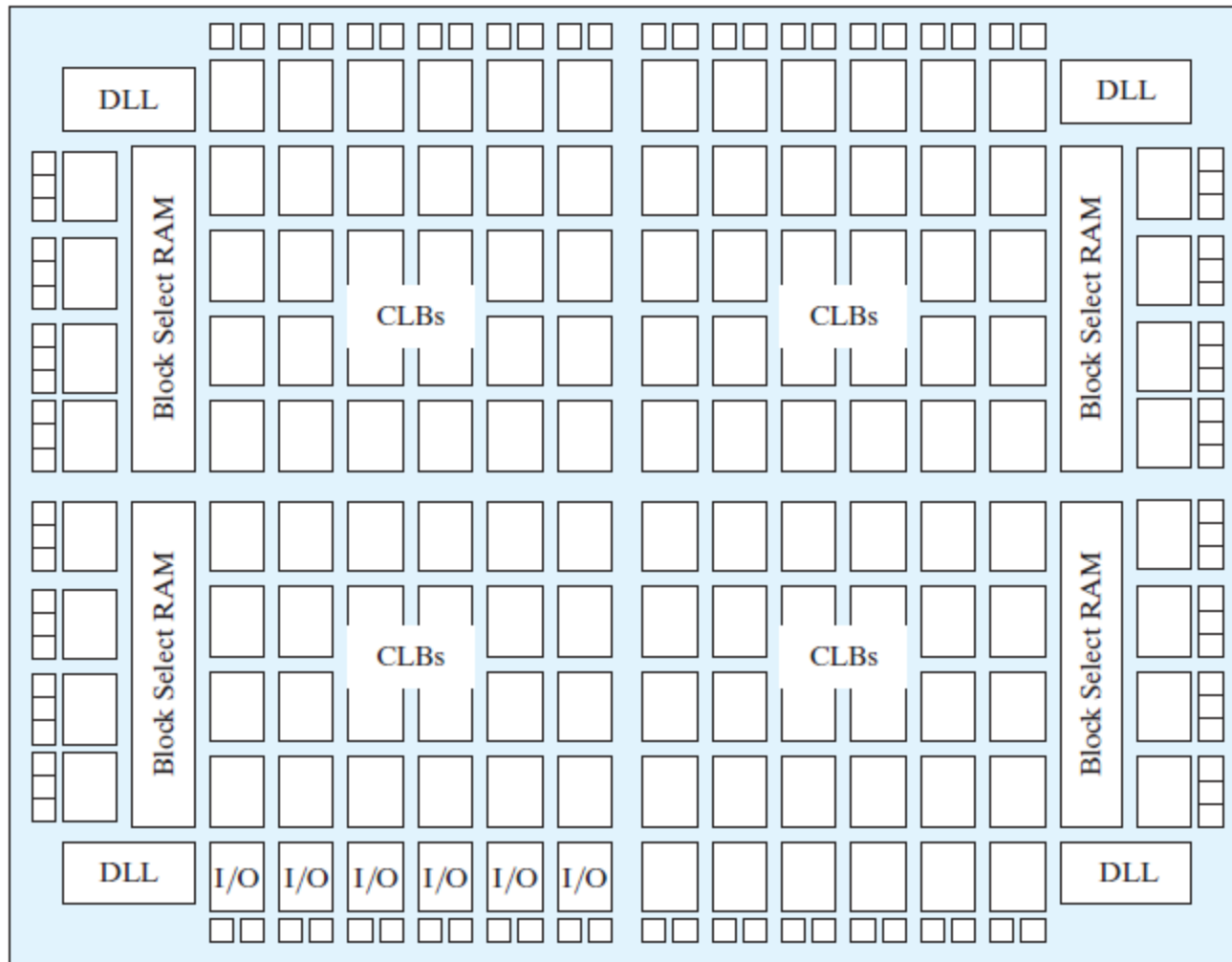


**FIGURE 7.28**  
Spartan II architecture

# FPGA

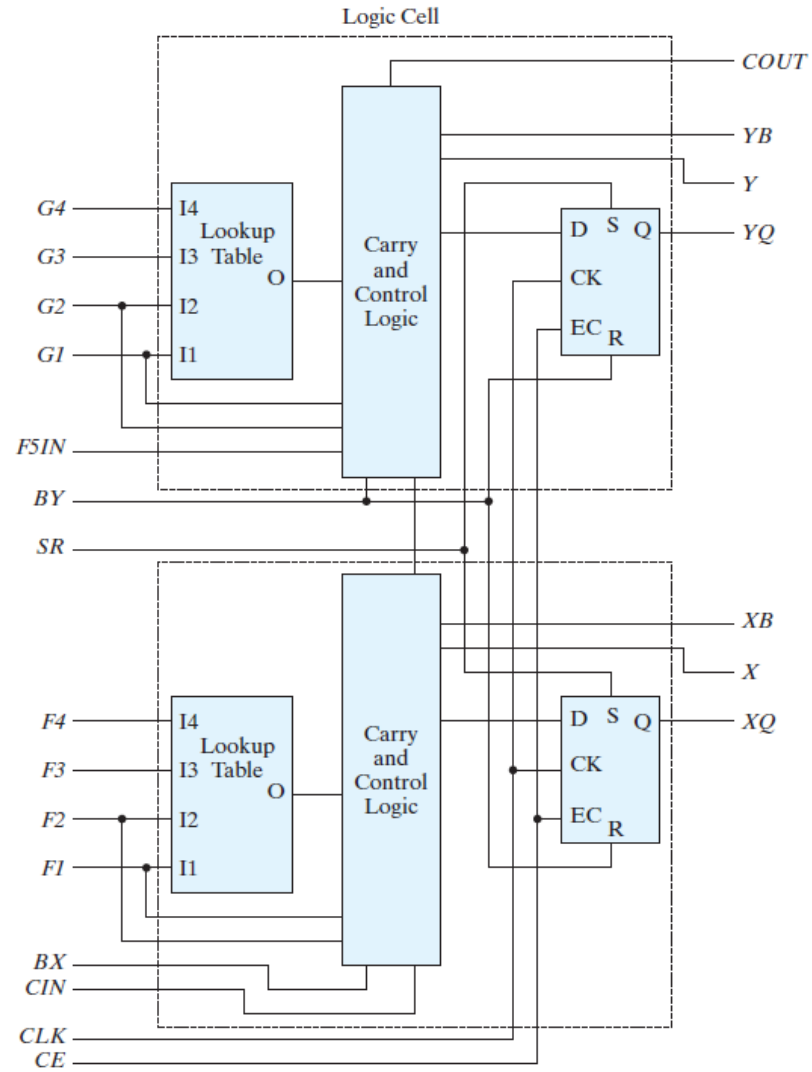

**FIGURE 7.29**  
Spartan II CLB slice

## FPGA

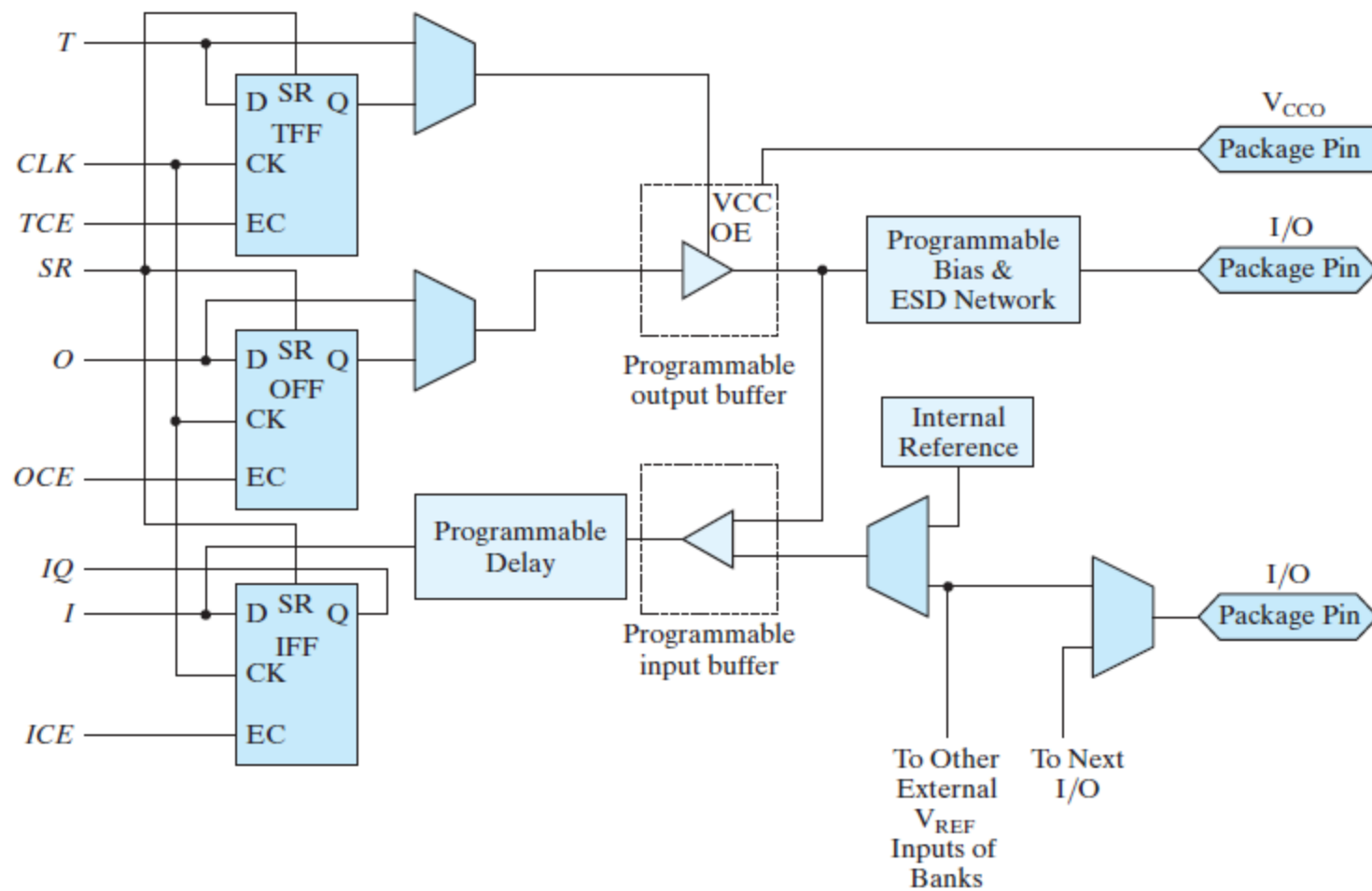

**FIGURE 7.30**  
Spartan II IOB

# VHDL

El lenguaje de programación **VHDL** (**V**ery **H**igh Speed Integrated Circuit **H**ardware **D**escription **L**anguage) es un lenguaje que describe el comportamiento del circuito, es decir describe el hardware

En la Fig 1 se observan los tres estilos de descripción

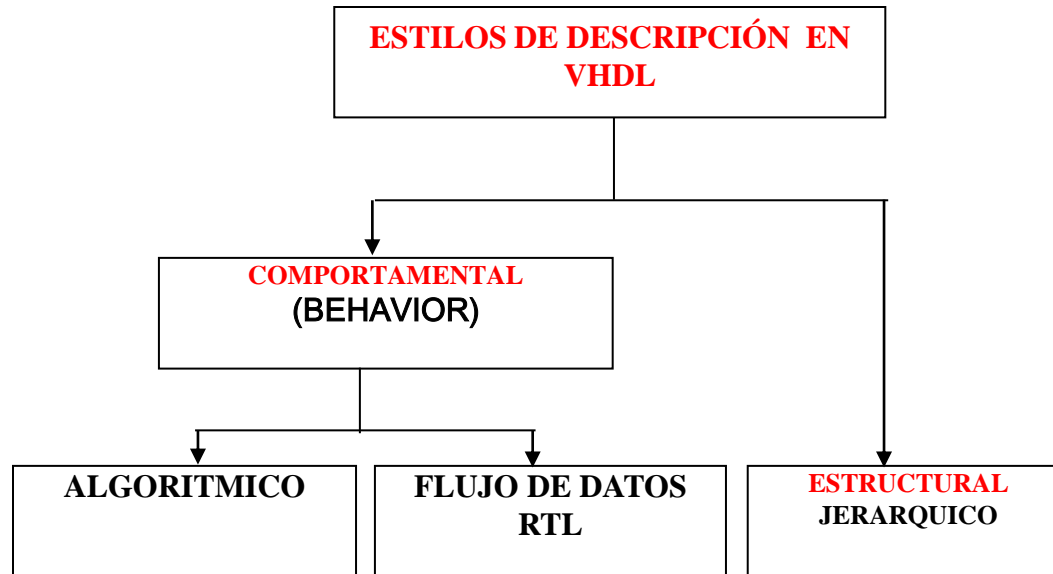


Fig. 1 Estilos de descripción VHDL

**VHDL – Lenguaje para síntesis y modelado de circuitos – Fernando Pardo y Jose Boluda**

**Editorial Alfaomega**

**VHDL - David Maxinez - Editorial C.E.C.S.A**

**Diseño de sistemas con VHDL – Editorial Paraninfo**

# VHDL

## ESTRUCTURA BASICA DE UN ARCHIVO FUENTE VHDL

ENCABEZAMIENTO	<b>Library</b> <nombre_libreria> <b>Use</b> <nombre_librería>.<nombre_paquete>. <b>all</b>
ENTIDAD	<b>Entity</b> <nombre_entidad> <b>is</b> <listado de puertos> --Declaración de pines <b>end</b> <nombre_entidad>;
ARQUITECTURA	<b>Architecture</b> <nombre_arquitectura> <b>of</b> <nombre_entidad> <b>is</b> --Declaracion de señales internas --Declaracion de tipos de datos definidos por el usuario --Declaracion de componentes en caso de instanciación <b>begin</b> --Cuerpo de la arquitectura --Se define la funcionalidad del diseño con: --Asignaciones concurrentes --Procesos --Instanciación de componentes <b>end</b> <nombre_arquitectura>;

## ENTIDAD Y ARQUITECTURA

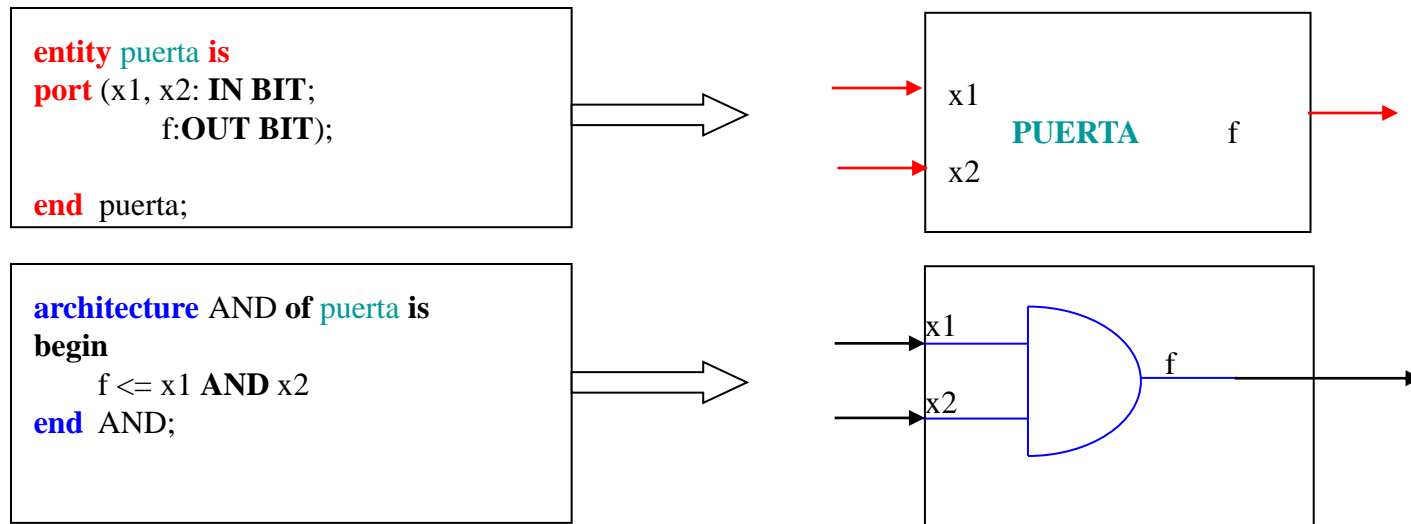


Fig. 4 Entidad y Arquitectura

## PUERTOS:

**IN:** ESTE PUERTO (DE ENTRADA) SE PUEDE SOLO **LEER** NUNCA ESCRIBIR

**OUT:** ESTE PUERTO (DE SALIDA) SE PUEDE SOLO **ESCRIBIR** NUNCA LEER, EL VALOR DE LA SEÑAL NO PUEDE USARSE DENTRO DE LA ENTIDAD

**INOUT:** (ENTRADA-SALIDA) PERMITE **LECTURA Y ESCRITURA**

**BUFFER:** (SALIDA) PERMITE **LECTURA Y ESCRITURA**, EL VALOR DE LA SEÑAL PUEDE USARSE DENTRO DE LA ENTIDAD



**ENTITY** ejemplo2 **IS**

**PORT** (x1, x2, x3, x4 : **IN** BIT;

f,g : **OUT** BIT);

**END** ejemplo2;


**ARCHITECTURE** LogicFunc **OF** ejemplo2 **IS**

**BEGIN**

f <= (x1 AND x3) OR (NOT x3 AND x2);

g <= (NOT x3 OR x1) AND (NOT x3 OR x4);

**END** LogicFunc;

 

- STD\_LOGIC
- STD\_LOGIC\_VECTOR
- SIGNAL

- IEEE 1164

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

- STD\_LOGIC

`PACKAGE std_logic_1164 IS`


```

-----
-- logic state system  (unresolved)
-----
TYPE std_ulogic IS ( 'U', -- Uninitialized
                     'X', -- Forcing  Unknown
                     '0', -- Forcing  0
                     '1', -- Forcing  1
                     'Z', -- High Impedance
                     'W', -- Weak      Unknown
                     'L', -- Weak      0
                     'H', -- Weak      1
                     '-'  -- Don't care
                     );

```

- **STD\_LOGIC\_VECTOR**

- **A : std\_logic\_vector(3 downto 0) | A : std\_logic\_vector(0 to 3)**

 


- **A(0) <='1';**
- **dato<=A(0) & A1 (3) & A1(5) ; -- Concatenación**

# VHDL SIGNALS

- **Signals:**
  - Se declaran dentro de la arquitectura.
  - Tienen las mismas propiedades que los puertos.
  - No salen fuera de la arquitectura.
  - Son cables y señales internas del dispositivo.
  - Se asignan igual que los puertos.
  - Son bidireccionales.
- **Declaracion**
- **<nombre>: tipo;**
- **D : std\_logic;**
- **D2: std\_logic\_vector(0 to 10);**
- **D3. std\_logic\_vector(10 downto 0)**

# VHDL SIGNALS

 

Entity compuerta is

Port ( A : in STD\_LOGIC;

B: STD\_LOGIC;

C: STD\_LOGIC;

OUT1 : OUT std\_logic;

OUT2. OUT std\_logic);

end compuerta;

# VHDL SIGNALS

**architecture Behavioral of compuerta is**

**Signal S1: std\_logic;**

**begin**

**out1<=S1;**

**S1<= A and B;**

**OUT2<= S1 and C;**

**end Behavioral;**

# VHDL STD\_LOGIC

IEEE 1164

LIBRARY IEEE;

USE IEEE.STD\_LOGIC\_1164.ALL;

STD\_LOGIC

```
PACKAGE std_logic_1164 IS
```


```
-----  
-- logic state system (unresolved)  
-----
```

```
TYPE std_ulogic IS ( 'U', -- Uninitialized  
                     'X', -- Forcing Unknown  
                     '0', -- Forcing 0  
                     '1', -- Forcing 1  
                     'Z', -- High Impedance  
                     'W', -- Weak Unknown  
                     'L', -- Weak 0  
                     'H', -- Weak 1  
                     '-' -- Don't care  
);
```

# VHDL STD\_LOGIC

## STD\_LOGIC\_VECTOR

A : STD\_LOGIC\_VECTOR(3 DOWNTO 0) | A :  
STD\_LOGIC\_VECTOR(0 TO 3)

 

A(0) <= '1';


DATO <= A(0) & A1(3) & A1(5); -- CONCATENACIÓN



# VHDL SIGNALS

- **Signals:**
    - Se declaran dentro de la arquitectura.
    - Tienen las mismas propiedades que los puertos.
    - No salen fuera de la arquitectura.
    - Son cables y señales internas del dispositivo.
    - Se asignan igual que los puertos.
    - Son bidireccionales.
  - **Declaración**
    - `<nombre>: tipo;`
- 
- `D : std_logic;`
  - `D2: std_logic_vector(0 to 10);`
  - `D3. std_logic_vector(10 downto 0)`

# VHDL SIGNALS

 

Entity compuerta is

Port ( A : in STD\_LOGIC;

B: STD\_LOGIC;

C: STD\_LOGIC;

OUT1 : OUT std\_logic;

OUT2. OUT std\_logic);

end compuerta;

# VHDL SIGNALS

architecture Behavioral of compuerta is

Signal S1: std\_logic;

begin

out1<=S1;


S1<= A and B;

OUT2<= S1 and C;


end Behavioral;

---

# VHDL – ISE TEMPLATES

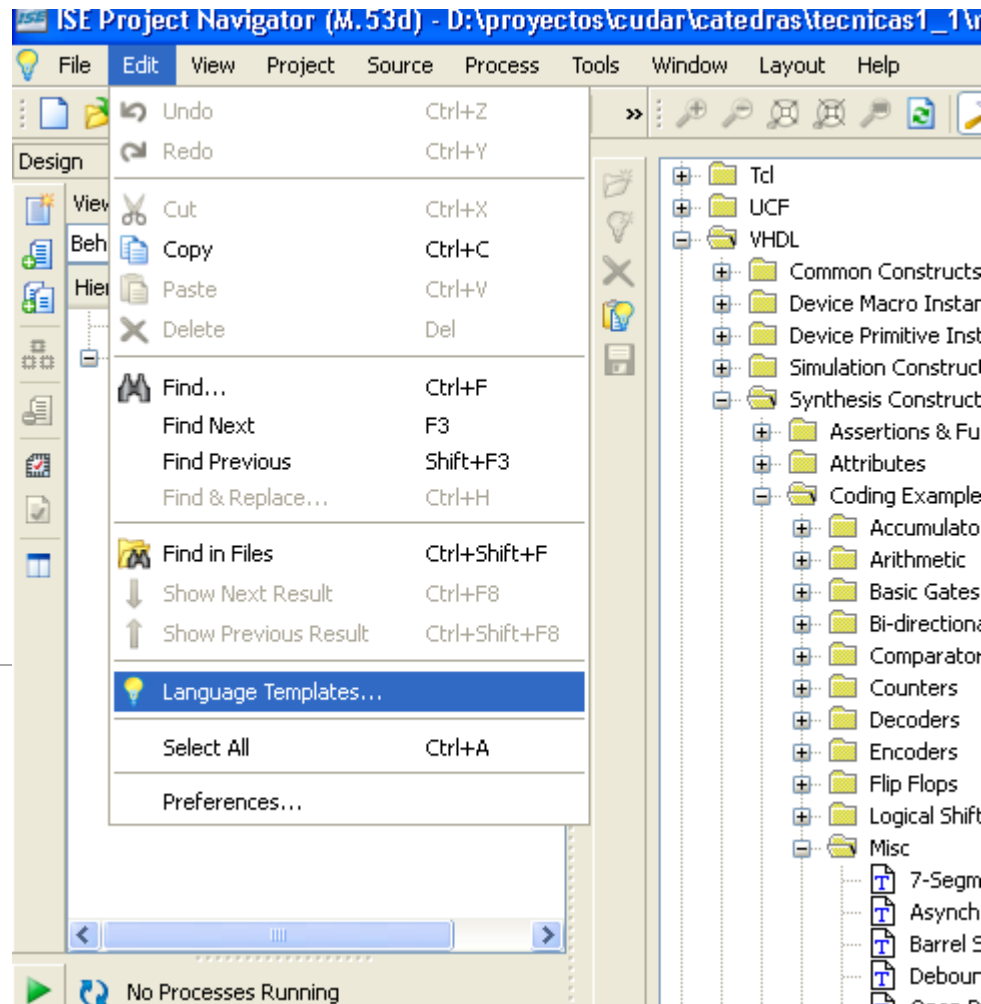

# VHDL – ISE TEMPLATES

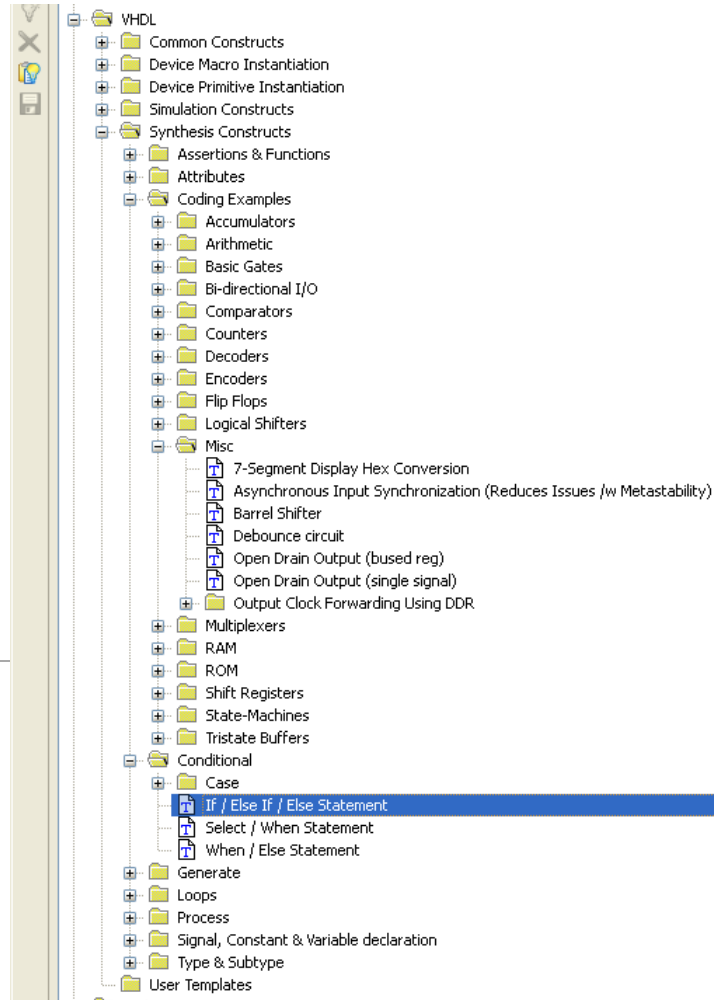

# TEMPLATE

```
WITH <CHOICE_EXPRESSION> SELECT  
  <NAME> <= <EXPRESSION> WHEN <CHOICES>,  
    <EXPRESSION> WHEN <CHOICES>,  
    <EXPRESSION> WHEN OTHERS;
```

---

# TEMPLATE BCD-7SEG

WITH HEX SELECT

```
LED<= "1111001" WHEN "0001",  --1
```

```
"0100100" WHEN "0010",  --2
```

```
"0110000" WHEN "0011",  --3
```

```
"0011001" WHEN "0100",  --4
```

```
"0010010" WHEN "0101",  --5
```

```
"0000010" WHEN "0110",  --6
```

```
"1111000" WHEN "0111",  --7
```

```
"0000000" WHEN "1000",  --8
```

```
"0010000" WHEN "1001",  --9
```

```
"0001000" when "1010",  --A
```

```
"0000011" when "1011",  --b
```

```
"1000110" when "1100",  --C
```

```
"0100001" when "1101",  --d
```

```
"0000110" when "1110",  --E
```

```
"0001110" when "1111",  --F
```

```
"1000000" when others;  --0
```

---


# Entidad

ENTITY BCD\_7SEGMENT IS

PORT ( ENTRADA : IN STD\_LOGIC\_VECTOR (3 DOWNT0 0);

SALIDA : OUT STD\_LOGIC\_VECTOR (6 DOWNT0 0));

END BCD\_7SEGMENT;

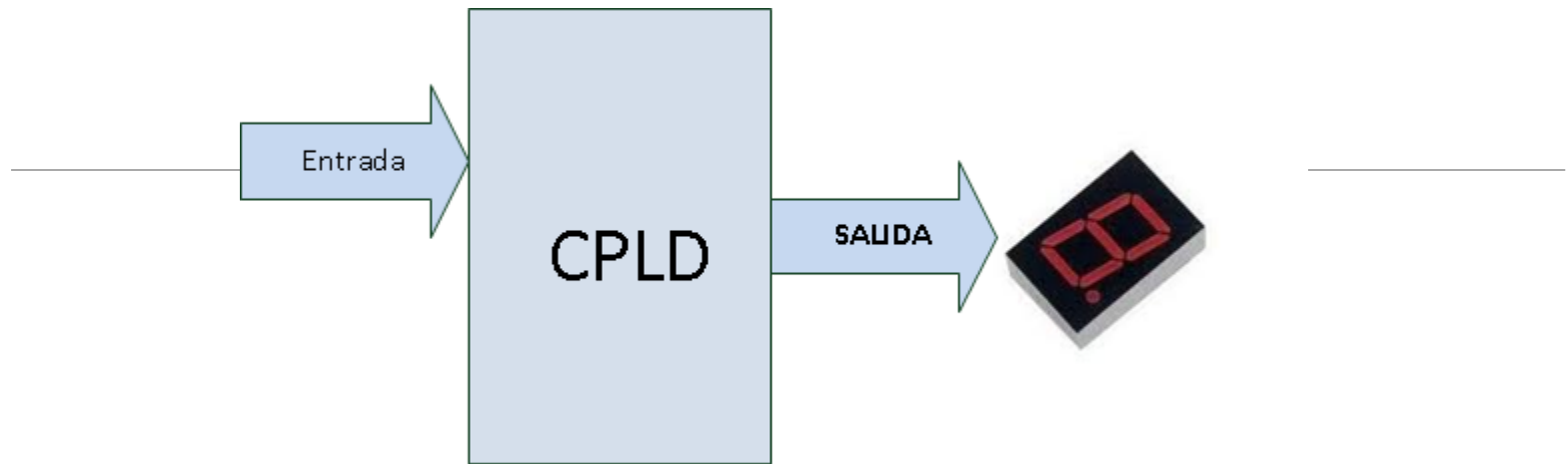



# Arquitectura

ARCHITECTURE BEHAVIORAL OF BCD\_7SEGMENT IS

BEGIN

WITH ENTRADA SELECT

SALIDA<= "1111001" WHEN "0001", --1

"0100100" WHEN "0010", --2

"0110000" WHEN "0011", --3

"0011001" WHEN "0100", --4

"0010010" WHEN "0101", --5

"0000010" WHEN "0110", --6

"1111000" when "0111", --7

"0000000" when "1000", --8

"0010000" when "1001", --9

"0001000" when "1010", --A

"0000011" when "1011", --b

"1000110" when "1100", --C

"0100001" when "1101", --d

"0000110" when "1110", --E

"0001110" when "1111", --F

"1000000" when others; --0

end Behavioral;

---

# when - else

```
<NAME> <= <EXPRESSION> WHEN <CONDITION> ELSE  
    <EXPRESSION> WHEN <CONDITION> ELSE  
    <EXPRESSION>;
```

---

# Arquitectura

ARCHITECTURE BEHAVIORAL OF BCD\_7SEGMENT IS

BEGIN

SALIDA<= "1111001" WHEN ENTRADA="0001" ELSE --1

"0100100" WHEN ENTRADA="0010" ELSE --2

"0110000" WHEN ENTRADA="0011" ELSE --3

"0011001" WHEN ENTRADA="0100" ELSE --4

"0010010" WHEN ENTRADA="0101" ELSE --5

"0000010" WHEN ENTRADA="0110" ELSE --6

"1111000" WHEN ENTRADA="0111" ELSE --7

---

"0000000" WHEN ENTRADA="1000" ELSE --8

"0010000" WHEN ENTRADA="1001" ELSE --9

"1000000" ; --0

END BEHAVIORAL;

# Rtl schematic

